
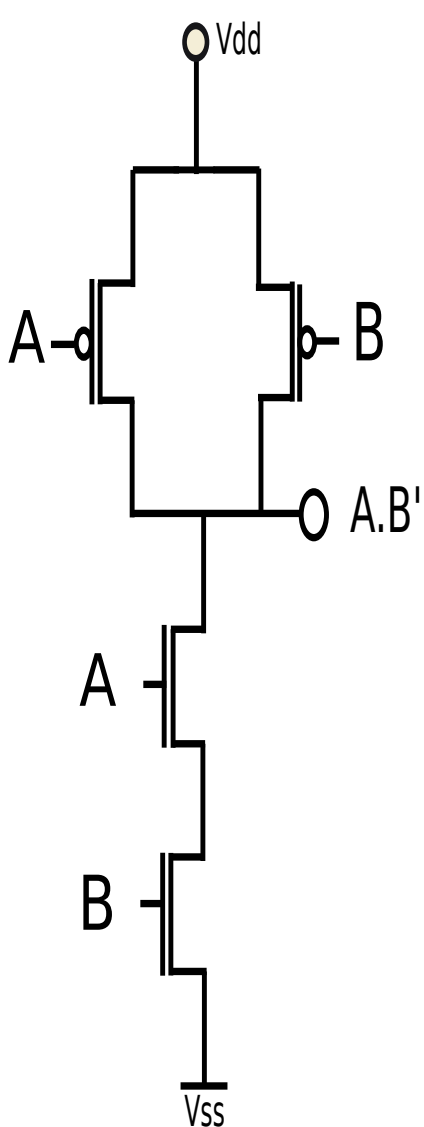


Inverter

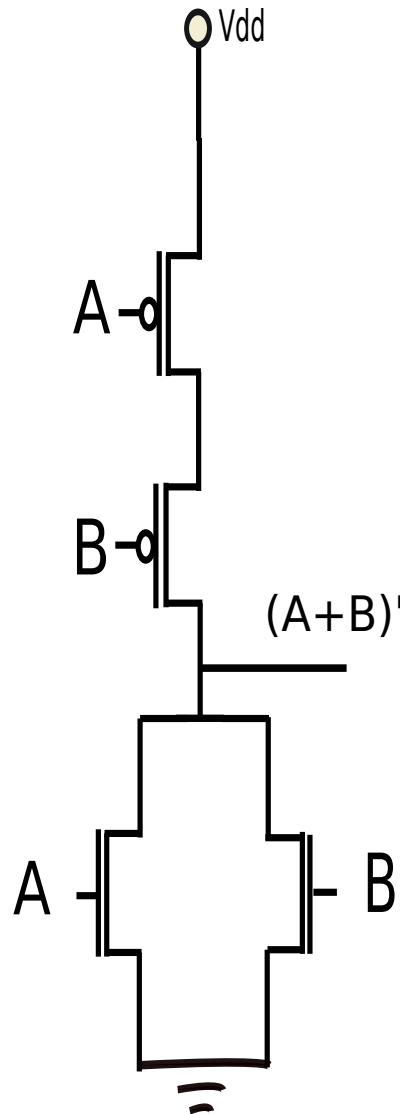

NAND



NOR